

*IEEE ASUSB AIC Winter  
Workshop 2025 - LAB 4*

## Part 1: Sizing Chart


We want to design a differential amplifier with the specifications below (listed in lab instructions file). Note that the bias current is split between two transistors; each transistor gets  $I_D = 20\mu A$ . Choose  $R_D$  to meet the CM output level spec.

$$\text{Given } I_D = 20\mu A, V_{O,CM} = V_{R_D} = 0.7V \rightarrow R_D = \frac{V_{R_D}}{I_D} = 35k\Omega.$$

Choose  $V^*$  to meet the differential gain spec.

$$\text{Given } A_{vd} = \frac{2V_{R_D}}{V^*} = 8, V_{R_D} = 0.7V \rightarrow V^* = 175mV.$$

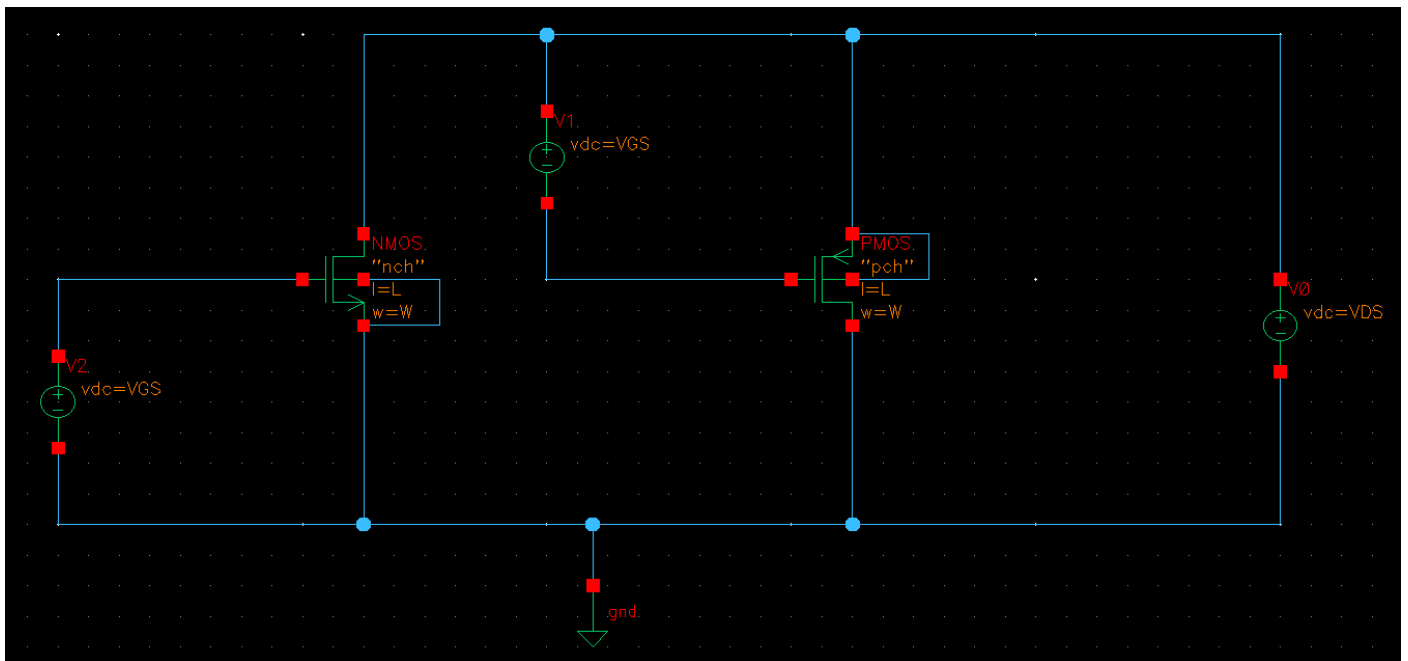
The remaining variable in the design is to calculate  $W$ . Since the square-law is not accurate, we cannot use it to determine the sizing. Instead, we will use a sizing chart generated from simulation. Create a testbench for PMOS transistor as shown below (we will use PMOS only in this lab). Use  $W = 10\mu m$  (we will understand why shortly).



Required testbench


Sweep  $V_{GS}$  from 0 to  $\sim V_{th} + 0.4V$  with 10mV step. Set  $V_{DS} = \frac{V_{DD}}{2}$ . We want to compare  $V^* = \frac{2I_D}{g_m}$  and  $V_{OV} = V_{GS} - V_{th}$  by plotting them overlaid. Use the calculator to create expressions for  $V^*$  and  $V_{OV}$ . You can save the expressions to reuse them later. Plot  $V^*$  and  $V_{OV}$  overlaid vs  $V_{GS}$ . Make sure the y-axis of both curves has the same range. On the  $V^*$  and  $V_{OV}$  chart locate the point at

 which  $V^*$  is equal to the value you previously calculated to meet the gain spec. Find the corresponding  $V_{OVQ}$  and  $V_{GSQ}$ .



Required plot with a cursor positioned at required region

 Plot  $I_D$ ,  $g_m$ , and  $g_{ds}$  vs  $V_{GS}$ . Find their values at  $V_{GSQ}$ . Let's name these values  $I_{DX}$ ,  $g_{mX}$ , and  $g_{dsX}$ .



$I_D$ ,  $g_m$  and  $g_{ds}$  VS  $V_{GS}$

Now back to the assumption that we made that  $W = 10\mu\text{m}$ . This is not the actual value that we will use for our design. But the good news is that  $I_D$  is always proportional to  $W$  irrespective of the operating region and the model of the MOSFET (regardless square-law is valid or no). Thus, we can use ratio and proportion (cross-multiplication) to determine the correct width at which the current will be  $I_{DQ}$  as given in the specs. Calculate  $W$  as shown below (in lab instructions file).

$W_X = 10\mu\text{m}$	$I_{DX} = 9\mu\text{A}$
$W_Q = ??$	$I_{DQ} = 20\mu\text{A}$

$$W_Q \approx 22\mu\text{m}.$$

Now we are almost done with the design of the amplifier. Note that  $g_m$  is also proportional to  $W$  as long as  $V_{OV}$  is constant. On the other hand,  $r_o = \frac{1}{g_{ds}}$  is **inversely** proportional to  $W$  ( $I_D$ ) as long as  $L$  is constant. Before leaving this part, calculate  $g_{mQ}$  and  $g_{dsQ}$  using ratio and proportion (cross-multiplication).

$W_X = 10\mu m$	$g_{mX} = 103\mu S$
$W_Q = 22\mu m$	$g_{mQ} = ??$

$$g_{mQ} \approx 227\mu S.$$

$W_X = 10\mu m$	$g_{dsX} = 740nS$
$W_Q = 22\mu m$	$g_{dsQ} = ??$

$$g_{dsQ} \approx 1.6\mu S.$$


## Part 2: Differential Amplifier

Create a new cell for the diff amp "lab\_04\_diff\_amp".

Create the schematic of a differential amplifier with PMOS input stage and resistive load.


Use a simple current mirror for the bias current source as shown in the first figure in this document.

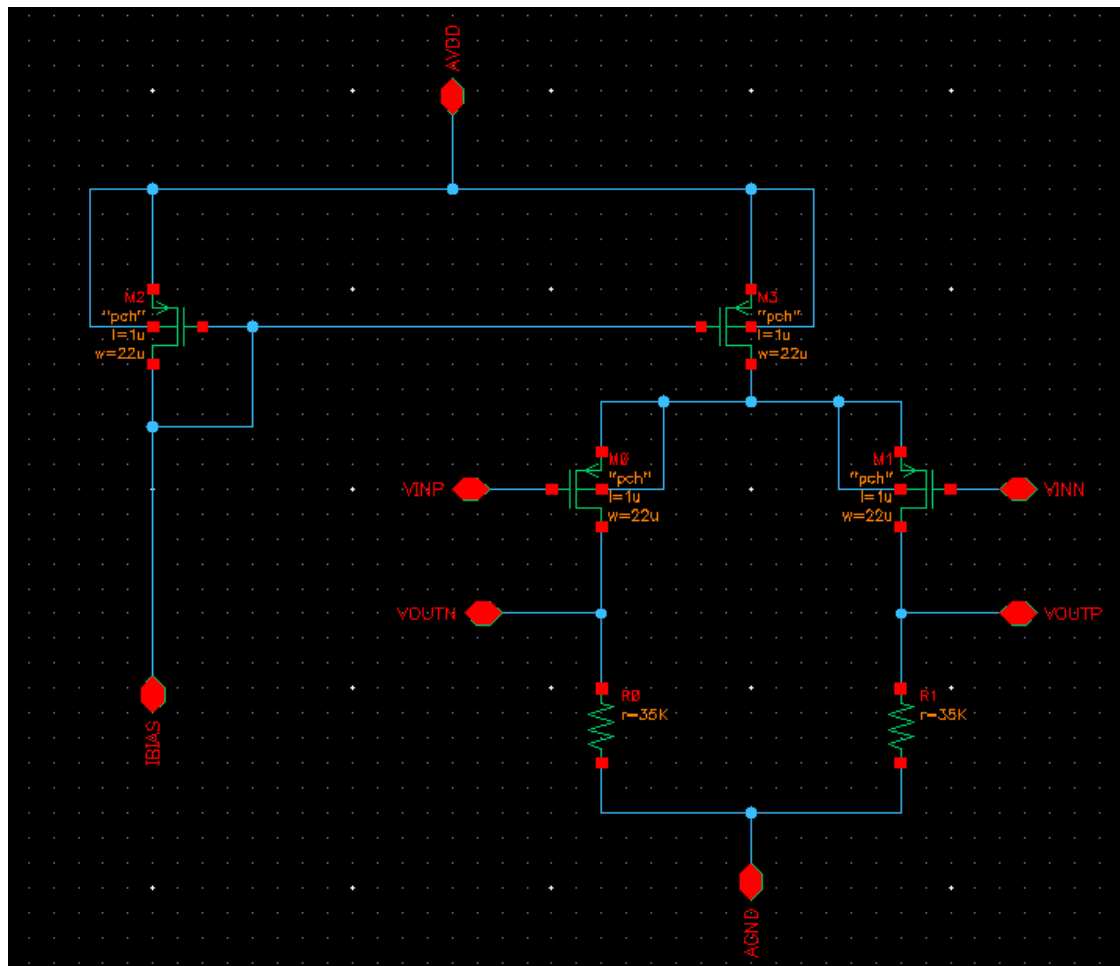Create a symbol for the diff pair (use Create -> Cellview -> From Cellview). Edit the diff amp symbol to be as shown below.



*Required schematic*

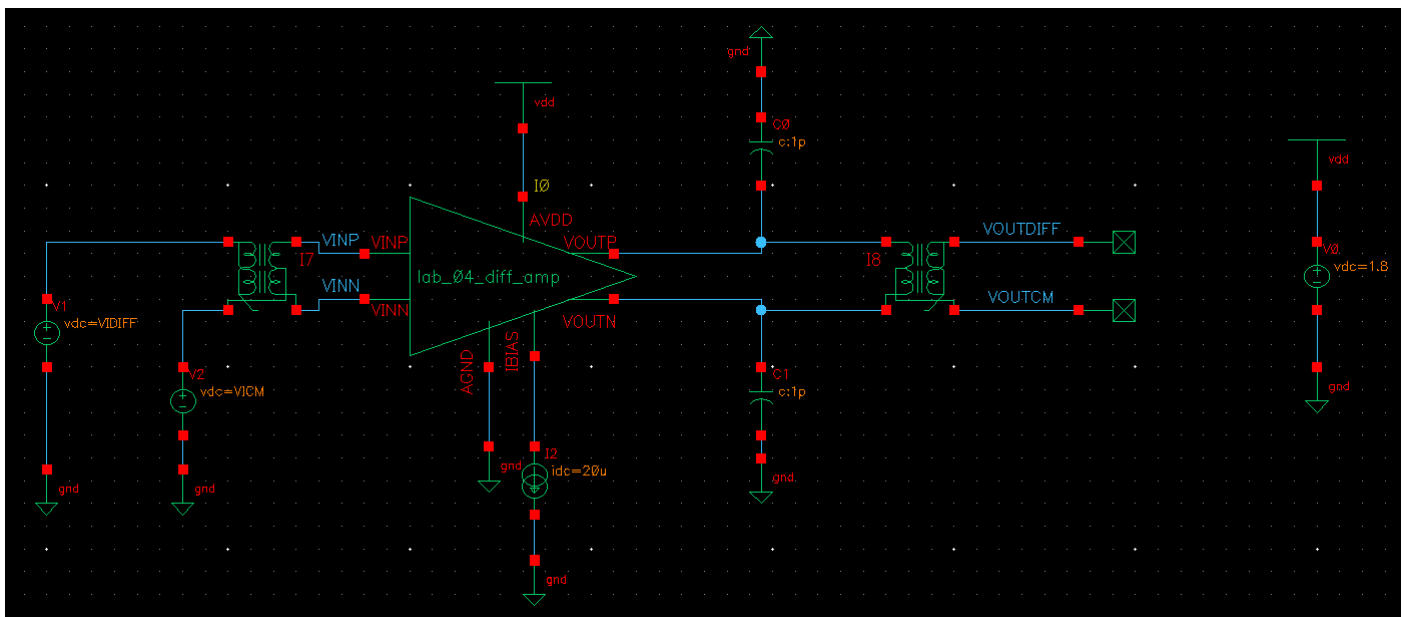Create a new cell for the testbench “lab\_04\_diff\_amp\_tb”. Create testbench schematic as shown below.



### Required testbench

Analytically calculate the valid range for  $V_{icm}$ : the common mode input range (CMIR). Set  $V_{icm}$  at the center of this range.

$$V_{DD} - V_{Dsat} > V_{iCM} > V_{oCM} - |V_{th}|$$

$$V_{DD} - V_{Dsat} \sim V_{DD} - V^* = 1.8V - 175mV = 1.625V.$$

$$V_{oCM} - |V_{th}| \approx 0.7 - 0.4 = 300mV.$$

$$1.625V > V_{iCM} > 300mV.$$


$$V_{iCM} = \frac{0.3 + 1.625}{2} \approx 960mV.$$

*Report the following:*

→ *OP simulation*

*Report the schematic of the diff pair with DC OP point clearly annotated: id, vgs, vds, vth, vdsat, gm, gds, gmb, region.*

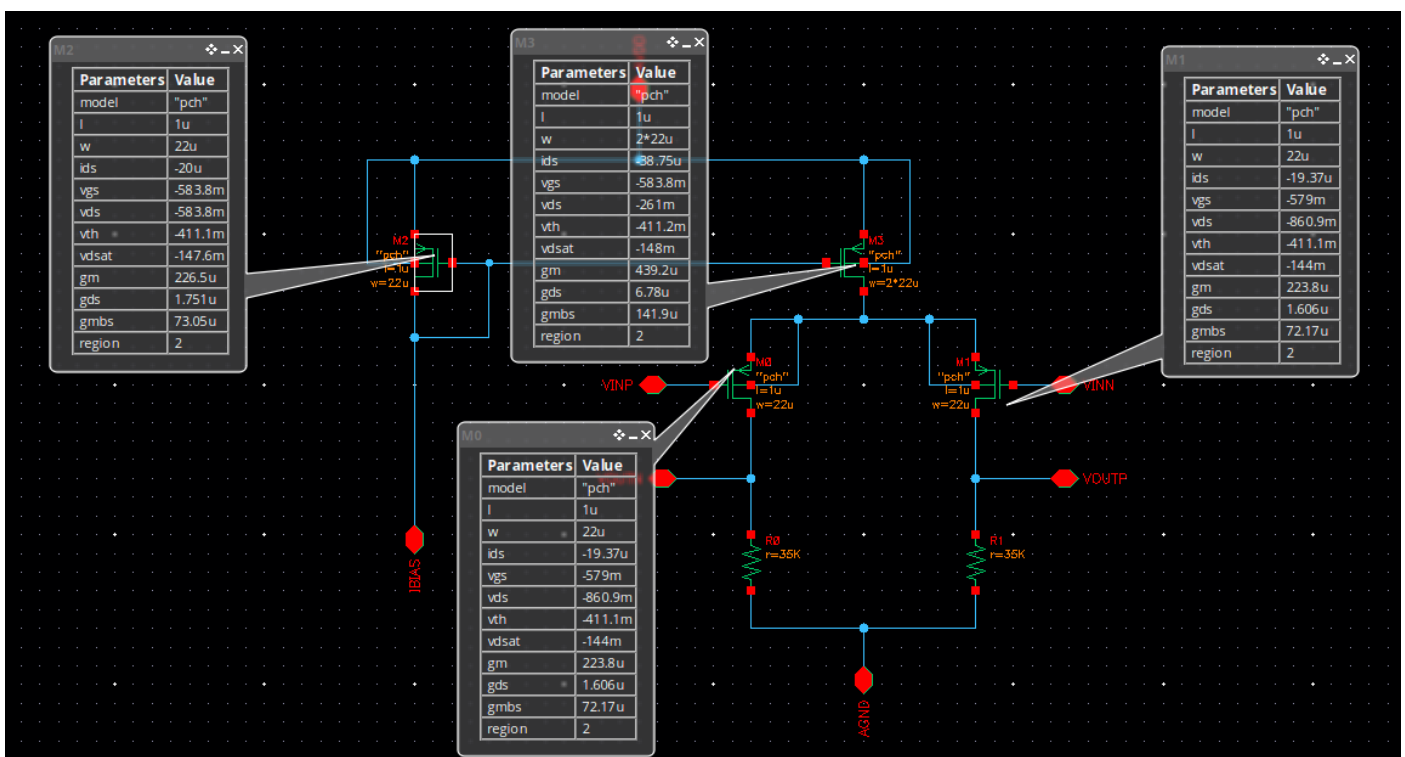*Check that all transistors operate in saturation.*



*Required snapshot*

- All transistors are operating in saturation, as indicated by "region" slot in the balloons.


→ *Diff small signal ccs*

*Use AC magnitude = 1 for the diff source (and AC magnitude = 0 for the CM source).*

*Set Vicm at the center of the CMIR.*

*Run AC analysis (1Hz:10GHz, logarithmic, 10 points/decade).*

 *Report the Bode plot of small signal diff gain.*



Bode mag plot of small signal diff gain

Compare the DC diff gain and BW with hand analysis in a table.


Quantity	Simulated	Calculated
DC gain	$\approx 17.5\text{dB}$	$\sim g_m R_D \approx 225\mu * 35k$ $= 7.9 = 17.9\text{dB}$
BW	$\approx 4.7\text{MHz}$	$\approx \frac{1}{2\pi R_D C_L}$ $= \frac{1}{2\pi * 1p * 35k} \approx 4.54\text{M}$

### → CM small signal ccs

Use AC magnitude = 1 for the CM source (and AC magnitude = 0 for the diff source).

Run AC analysis (1Hz:10GHz, logarithmic, 10 points/decade).

 Report the Bode plot of small signal CM gain.



Bode mag plot of small signal CM gain

Compare the DC CM gain with hand analysis in a table. Is it smaller than “1”? Why?


Simulated	Calculated
-18.7dB	$= \frac{g_m R_D}{1 + 2g_{me} R_{SS}} \approx 0.088 = -21dB$

- It IS smaller than 1 due to half circuit principle that resulted in a large amount of degeneration in CM compared to diff operation.

Justify the variation of  $A_{vCM}$  vs frequency.

- The presence of capacitors connected to the o/p is translated into an o/p impedance which is frequency dependent, and this, in turn, affects the gain when frequency changes as the gain is a function of o/p impedance.

 Plot  $A_{vd}/A_{vcm}$  in dB. Compare  $A_{vd}/A_{vcm}$  @ DC with hand analysis in a table.



Required plot

Simulated	Calculated
35dB	$1 + 2g_m R_{SS} \approx 67.4 = 36.6dB$

Justify the variation of  $A_{vd}/A_{vcm}$  with frequency.


- The presence of capacitors connected to the o/p is translated into an o/p impedance which is frequency dependent, and this, in turn, affects the gain when frequency changes as the gain is a function of o/p impedance.


 
### → Diff large signal ccs

Use dc sweep (not parametric sweep) for  $V_{id} = -V_{DD}:10m:V_{DD}$ . Set  $V_{icm}$  at the center of the CMIR.

Report diff large signal ccs ( $V_{ODIFF}$  vs  $V_{IDIFF}$ ). Compare the extreme values with hand analysis in a table.



Differential large signal CCs

Simulated	Calculated
$\pm 1.4V$	$= \pm I_{SS} R_D = 40\mu * 35k = \pm 1.4V$

### → CM large signal ccs (region vs $V_{ICM}$ )

We will use the region parameter to know the operating region of each transistor vs sweep variable.

Use DC sweep (not parametric sweep) for  $V_{icm} = 0:10m:V_{DD}$  (no need to run AC sim). Disable ac analysis.

Plot “region” OP parameter vs  $V_{ICM}$  for the input pair and the tail current source.



Required plot. The different plot is of the tail CS

Find the CM input range (CMIR). Compare with hand analysis in a table.


- CMIR can be inferred from the previous plot by noticing the voltage range corresponding to the input pair being operated in region 2 (sat).

Simulated	Calculated
$0.3V < CMIR < 1.4V$	$0.3V < CMIR < 1.625V$
 
### → CM large signal ccs (GBW vs Vicm)


Use ac analysis (start = 1, stop = 1, pts(linear) = 1) to get  $A_{vd}$ . Use parametric sweep (not dc sweep) for  $V_{icm} = 0:20m:V_{DD}$ .

Report CM large signal ccs ( $A_{vd}$  vs  $V_{icm}$ ). Assume the valid range for  $V_{icm}$  (CMIR) is defined by the condition that  $A_{vd}$  is within 90% of the max gain, i.e., 10% drop in gain.



$A_{vd}$  VS  $V_{iCM}$ . Employing 'ymax' function resulted in 7.458.

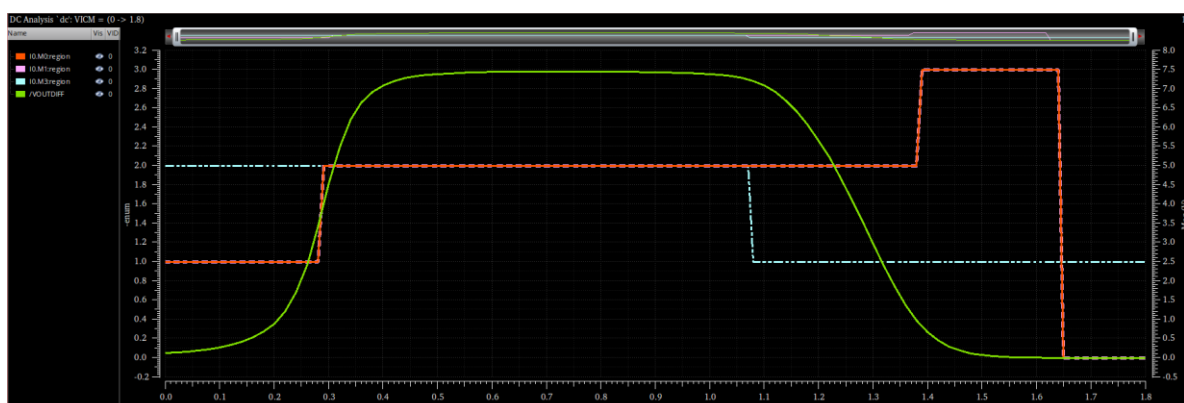Plot the results overlaid on the results of the previous method (region parameter). Find the CM input range. Compare with the previous method in a table.



Required plot overlaid with the results of the previous method

<i>Previous method</i>	<i>This method</i>
$0.3V < CMIR < 1.4V$	$10\% \text{ drop in } A_{vd} \rightarrow 0.9 * 7.458 = 6.7$ <i>(As indicated by V cursors added to the plot)</i> $365mV < CMIR < 1.14V$