

IEEE ASUSB AIC Design
Winter Workshop 2025
Final Project
5T OTA Design

Part 2: OTA Design


Use g_m/I_D methodology to design a diff input SE output operational transconductance amplifier (OTA) that achieves the following specs (listed in lab instructions file). Use an ideal external 10uA DC current source in your test bench (not included in the OTA current consumption spec), but design your own current mirror.

- I prefer not to use g_m/I_D design methodology. Rather the so called “cross multiplication” method is more suitable for me.


Report the following:

Detailed design procedure and hand analysis. You need to explain why you chose the architecture that you implemented.

- The **CMIR** spec indicates that the architecture that should be used is the one with **NMOS** input pair, as CMIR range is closer to V_{DD} .
- Let the initial guess of the channel length of the tail CS and CM load be something like 1um (long channel). Long channels provide higher r_o which translates into more ideal behavior expected from the tail CS (more tendency to act as an ideal current source) and mitigate the effect of V_{DS} variations on the ideality of current mirroring action when it comes to CM load.
- Let the initial guess of L of the input pair be, say 1 um. This choice seems to be somehow arbitrary. Most likely it would be fine-tuned.
- The reference W , i.e. W_X would be 10 um as usual.
- We may choose $V_{i/p}^*$ to be 200mV, namely the soft spot. In the MOS tb, V_{DS} will be set to 250mV to bias the i/p pair a little deeper into sat (note that V^* can be considered as a good estimation for V_{DSat}).

 

 $V_{OV,i/p}$ and $V_{i/p}^*$ VS V_{GS} . $V_{GSi/pQ} \approx 615mV$, $V_{OVi/pQ} = 206mV$.



The $I_{Di/p}$, $g_{mi/p}$ and $g_{dsi/p}$ VS V_{GS} and their values, $I_{Di/pX}$, $g_{mi/pX}$ and $g_{dsi/pX}$ at V_{GSQ} .

- My favorite part, the **Cross Multiplication**.

W

$W_X = 10\mu m$	$I_{Di/pX} = 45.5\mu A$
$W_{i/pQ} = ??$	$I_{Di/pQ} = 10\mu A$

$$W_{i/pQ} \approx 2.2\mu m.$$

g_m

$W_X = 10\mu m$	$g_{mi/pX} = 450\mu S$
$W_{i/pQ} = 2.2\mu m$	$g_{mi/pQ} = ??$


$$g_{mi/pQ} \approx 100\mu S.$$

g_{ds}


$W_X = 10\mu m$	$g_{dsi/pX} = 11.2\mu S$
$W_{i/pQ} = 2.2\mu m$	$g_{dsi/pQ} = ??$

$$g_{dsi/pQ} \approx 2.5\mu S, g_m r_O = \frac{g_m}{g_{ds}} \approx 40.6 < 50 \text{ (DC gain listed in specs sheet):}$$

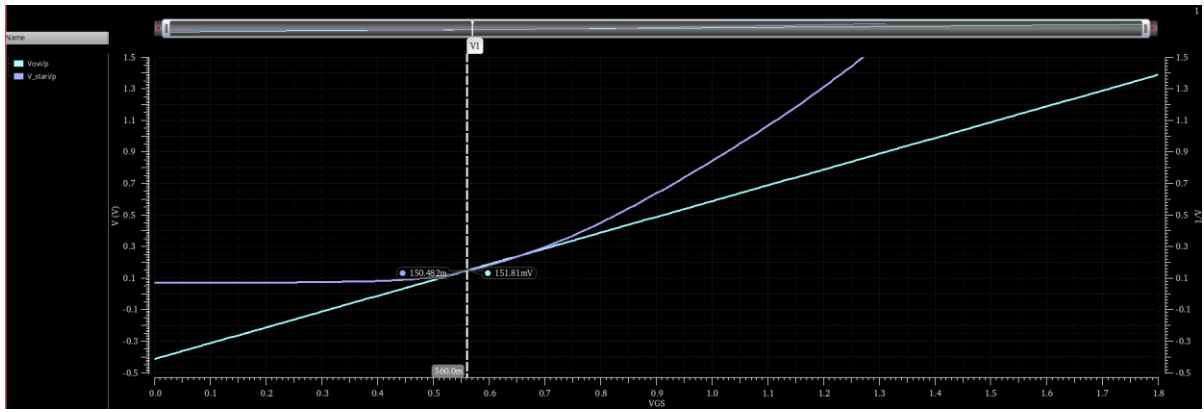- Reducing $V_{i/p}^*$ seems like a good decision as one of the alternatives is increasing V_{DS} which will waste headroom. The former is better when thinking this way. Let $V_{i/p}^* = 150mV$.



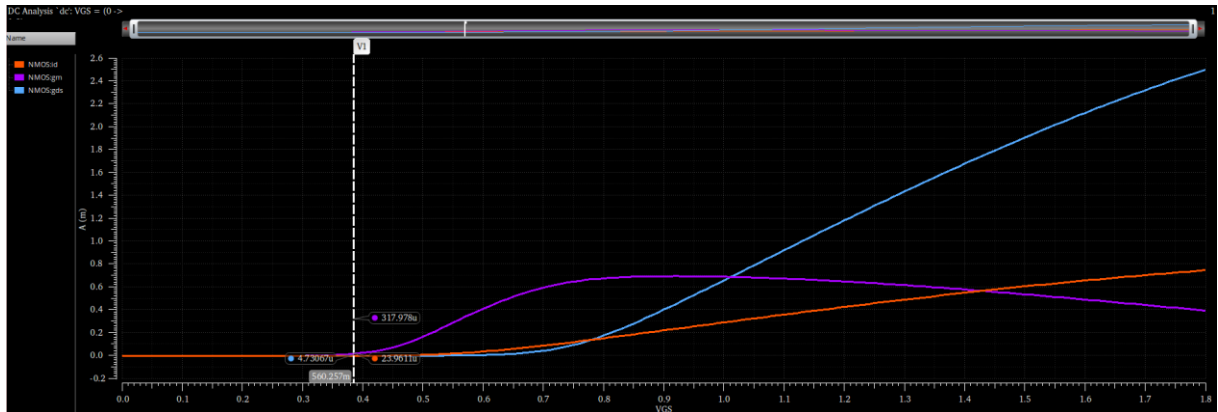$V_{OVI/p}$ and $V_{I/p}^*$ VS V_{GS} after refining V^* . $V_{GSI/pQ} \approx 560mV$, $V_{OVI/pQ} \approx 150mV$.



The $I_{Di/p}$, $g_{mi/p}$ and $g_{dsi/p}$ VS V_{GS} and their values, $I_{Di/pX}$, $g_{mi/pX}$ and $g_{dsi/pX}$ at V_{GSP} .

W

$W_X = 10um$	$I_{Di/pX} = 24uA$
$W_Q = ??$	$I_{Di/pQ} = 10uA$

$$W_{i/pQ} \approx 4.2um.$$

g_m

$W_X = 10um$	$g_{mi/pX} = 318uS$
$W_Q = 4.2um$	$g_{mi/pQ} = ??$

$$g_{mi/pQ} \approx 133uS.$$

g_{ds}


$W_X = 10um$	$g_{dsi/pX} = 4.7uS$
$W_Q = 4.2um$	$g_{dsNQ} = ??$

$$g_{dsNQ} \approx 2uS, g_m r_O = \frac{g_m}{g_{ds}} = 66.5 > 50 :D$$


- Let's design the tail current source. V_{tcs}^* would be determined from the lower limit of **CMIR**.

Applying KVL: $V_{iCMLo} - V_{Gsi/pQ} - V_{tcs}^* = 0$.
 Given $V_{Gsi/pQ} = 560mV$, $V_{iCMLo} = 0.8V \rightarrow V_{tcs}^* = 240mV$.

 - Current sources need the largest r_o possible. One essential parameter contributing in maximizing r_o is V_{DS} . In MOS tb, V_{DS} would be set to 300mV to go some distance deeper into sat.



 V_{ovtcs} and V_{tcs}^* VS V_{GS} . $V_{GstcsQ} \approx 653mV$, $V_{ovtcsQ} \approx 245mV$.



The I_{Dtcs} , g_{mtcs} and g_{dstcs} VS V_{GS} and their values, I_{DtcsX} , g_{mtcsX} and g_{dstcsX} at V_{GSQ} .

W


$W_X = 10\mu m$	$I_{DtcsX} = 64\mu A$
$W_Q = ??$	$I_{DtcsQ} = 20\mu A$

$W_{tcsQ} \approx 3.1\mu m$.


- It's time to move the attention to CM load. V_{CML}^* would be determined from the upper limit of **CMIR** spec.

Applying KVL: $V_{CML}^* = V_{DD} - V_{iCMHi} - |V_{THP}| + V_{THN}$.
 Given $V_{DD} = 1.8V$, $V_{iCMHi} = 1.5V$, $|V_{THP}| = 411mV$, $V_{THN} = 407mV$
 $V_{CML}^* = 297mV$. (V_{TH} data is obtained from DC OP)

 - Again, to go deeper into sat, V_{DS} would be set to 350mV in MOS tb.



 V_{OVCML} and V_{CML}^* VS V_{GS} . $V_{GSCMLQ} \approx 696mV$, $V_{OVCMLQ} \approx 285mV$.



The I_{DCML} , g_{mCML} and g_{dsCML} VS V_{GS} and their values, I_{DCMLX} , g_{mCMLX} and g_{dsCMLX} at V_{GSQ} .


W

$W_X = 10\mu m$	$I_{DCMLX} = 23.6\mu A$
$W_Q = ??$	$I_{DCMLQ} = 10\mu A$

$W_{CMLQ} \approx 4.2\mu m$.

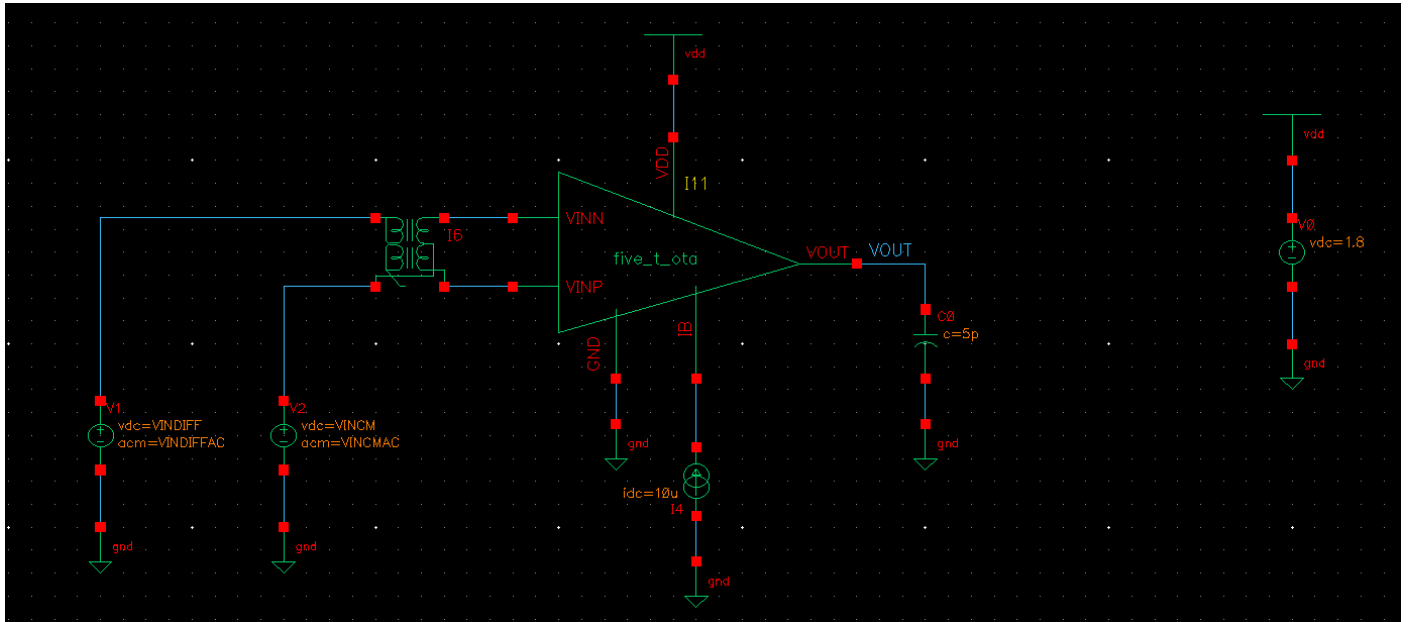Part 3: Open-Loop OTA Simulation


Create a testbench as shown above. Note that IDC connection (sinking or sourcing) in the test bench may be different from the one shown above depending on the type of your input pair (PMOS/NMOS).



Required schematic

Schematic of the OTA with DC node voltages clearly annotated.

- Use VICM at the middle of the CMIR.

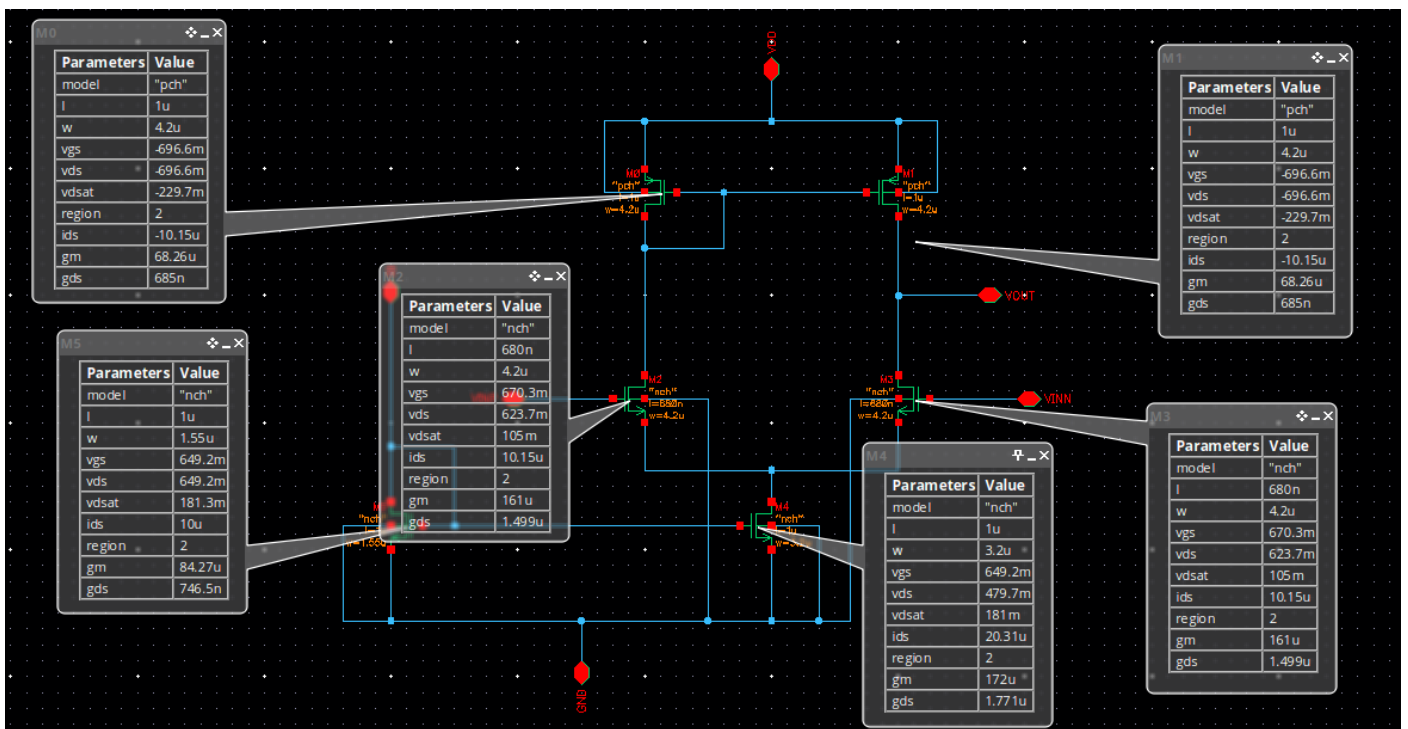

Required snapshot

- Is the current (and g_m) in the input pair **exactly** equal?

Yes.

- What is DC voltage at V_{OUT} ? Why?

$$V_{OCM} \approx 1.1 = \frac{V_{in1} + V_{in2}}{2} = V_{in1,2}$$


Diff small signal ccs:

- Use AC analysis (1Hz:10GHz, logarithmic, 10 points/decade).

Set $V_{IDAC} = 1$ and $V_{ICMAC} = 0$.

Use V_{ICM} at the middle of the $CMIR$.

Plot diff gain (in dB) vs frequency.

 

Bode mag plot of diff gain

Test	Output	Nominal	Spec	Weight	Pass/Fail
IEEE_ASUSB:five_t_ota_tb:1	Av_diff_mag	73.36			
IEEE_ASUSB:five_t_ota_tb:1	Av_diff_dB	37.31			
IEEE_ASUSB:five_t_ota_tb:1	BW	68.64k			
IEEE_ASUSB:five_t_ota_tb:1	UGF	5.033M			
IEEE_ASUSB:five_t_ota_tb:1	GBW	5.048M			

Required calculations

- Compare simulation results with hand calculations in a table.

Quantity	Simulated	Calculated
DC gain	73.4	$g_{m12}(r_{o2} r_{o4}) \approx 73.7$
BW	68.6kHz	$\frac{1}{2\pi R_{out} C_L} \approx 69.6kHz$
GBW	5.048MHz	5.12MHz


CM small signal ccs:

- Use AC analysis (1Hz:10GHz, logarithmic, 10 points/decade).

Set $VICMAC = 1$ and $VIDAC = 0$.

Use $VICM$ at the middle of the $CMIR$.

Plot CM gain in dB vs frequency.

 

Bode Mag plot of CM gain


- Compare simulation results with hand calculations in a table.

Quantity	Simulated	Calculated
A_{vCM}	$\approx -40dB$	$\frac{g_{dstcs}}{2g_{m34}} \approx 13.2e - 3$ $= -37.6dB$

(Optional) A_{vcm} vs $VICM$:

- Use **parametric sweep** (not **DC sweep**) for $VICM = CMIR$ -low:10m:CMIR-high.

Plot CM gain at 1Hz in dB vs $VICM$.

 

Required plot


- Justify the results.

As V_{iCM} increases, V_{DStcs} increases in response. Thus, r_{Otcs} , or the so-called R_{SS} also increases. This R_{SS} is inversely proportional to A_{vCM} . This can be summarized as follows: $V_{iCM} \uparrow \rightarrow V_{DStcs} \uparrow \rightarrow R_{SS} \propto \frac{1}{A_{vCM}} \uparrow \rightarrow A_{vCM} \downarrow$.

CMRR:

- Use VICM at the middle of the CMIR.

 Plot CMRR in dB vs frequency at VICM at the middle of the CMIR.



Required plot


- Compare simulation results with hand calculations in a table.

Quantity	Simulated	Calculated
CMRR	77dB	$= A_{vddB} - A_{vCMdB}$ $\approx 77dB$

(Optional) CMRR vs VICM:

- Use **parametric sweep (not DC sweep)** for VICM = CMIR-low:10m:CMIR-high.

Plot CMRR at 1Hz in dB vs VICM.

 

Required plot

- Justify the results.


At V_{iCMLO} , V_{DStcs} is at its lowest limit and so is R_{SS} . Thus A_{vCM} is maximum as there is inverse proportionality between R_{SS} and A_{vCM} , as mentioned above. This can be related to the poor CMRR ($\max(A_{vCM}) \leftrightarrow \min(CMRR)$). Increasing V_{iCM} leads to A_{vCM} degradation and thus **CMRR** increases. When V_{iCM} approaches its maximum allowable value, CMRR begins to decrease since the i/p pair gets closer to the edge of sat which is a region characterized by poor g_m and r_o , and this corresponds to poor A_{vd} and thus poor CMRR.

Diff large signal ccs:

- Use VICM at the middle of the CMIR.


Use DC sweep (**not parametric sweep**) $VID = -VDD:1m:VDD$. You must use a small step (1mV) because the gain region is very small (steep slope).

 Plot V_{OUT} vs VID . From the plot, what is the value of V_{out} at $VID = 0$? Why?



Required plot

- $V_O(0) \approx 1.1V$. This value is the same as the one obtained in DC OP analysis, and they are similar since the inputs to the circuit in both cases are **exactly** the same. In DC OP analysis, the CM input was set to the middle of CMIR and so is the case here. Additionally, in the former analysis, no diff excitation was present and **so the case here** as $V_{id} = 0$.
- Plot the derivative of V_{OUT} vs VID . Compare the peak with A_{vd} .

 


Required plot

- $\max(\text{deriv}(A_{vd})) = 73 = A_{vd}$.

CM large signal ccs (region vs VICM):

 - Use **DC sweep** (not parametric sweep) $VICM = 0:10m:VDD$. Plot “region” OP parameter vs $VICM$ for the input pair and the tail current source (0 cut-off, 1 triode, 2 sat, 3 subth, and 4 breakdown). Plot the results overlaid on the results of the previous method (10% reduction of GBW).




Required plot. $Y_{\max}(V_{out})=76.35$, 10% reduction of V_{out} corresponds to $V_{out}=68.7$.

$0.8V < CMIR < 1.8V$ (from region data)
 $385mV < CMIR < 1.4V$ (from 10% gain drop data)

Part 4: Closed-Loop OTA Simulation


Create a testbench as shown above.

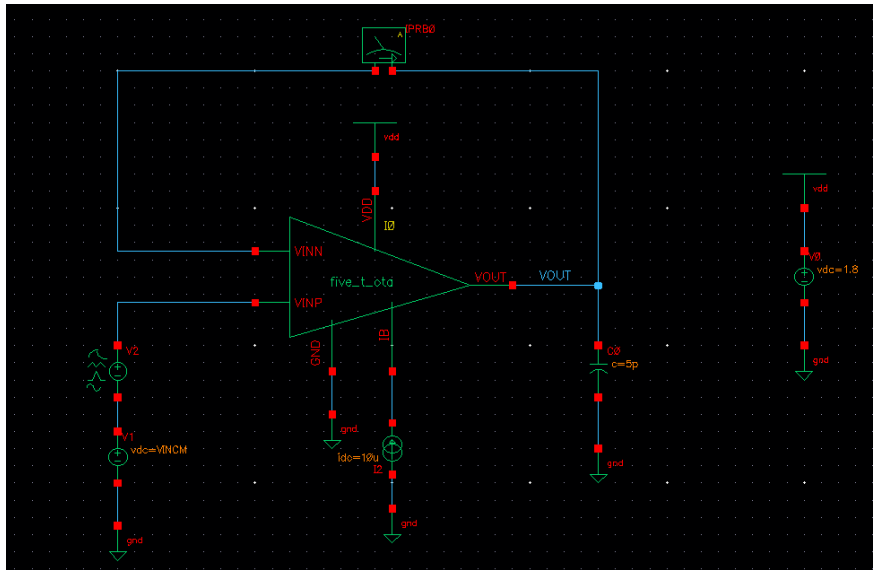

Required testbench

Report the following:

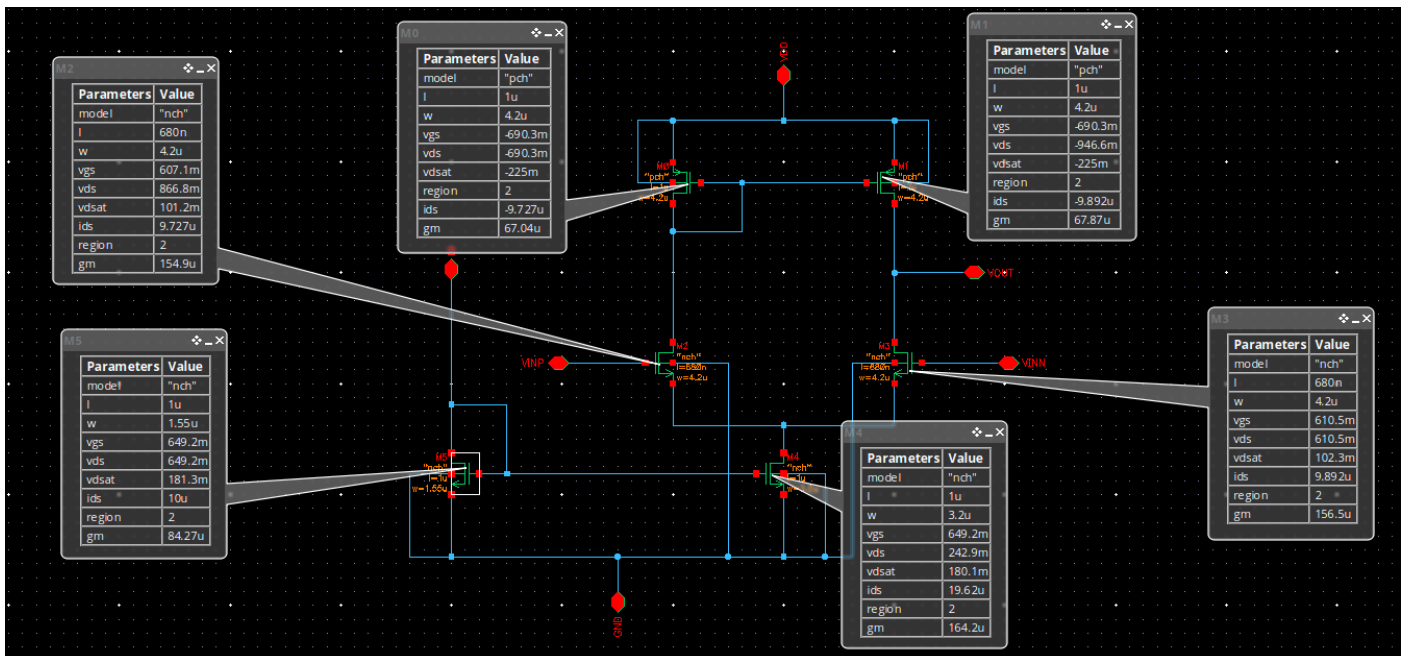- Schematic of the OTA with DC OP point clearly annotated in unity gain buffer configuration. Use $VIN = CMIR-low + 50mV$.



Required snapshot

- Is the current (and g_m) in the input pair exactly equal? Why?
No. There is a slight difference due to a similar difference in V_{GS} resulting from the finite practical (deviation from ideality) difference present between the inverting and non-inverting terminals of the OTA.

- Calculate the mismatch in I_D and g_m .

$$\% \Delta I_D = \frac{I_{DLeft} - I_{DRight}}{I_{DRight}} \approx 1.66\% \text{ (Assuming the right half is the ref)}$$


$$\% \Delta g_m = \frac{g_{mLeft} - g_{mRight}}{g_{mRight}} \approx 1.02\% \text{ (Assuming the right half is the ref)}$$

Loop gain:

- Use STB analysis (1Hz:10GHz, logarithmic, 10 points/decade) in unity gain buffer configuration.

Use VICM at the middle of the CMIR.

 Plot loop gain in dB and phase vs frequency.



Bode Mag and ϕ plots of loop gain

Test	Output	Nominal	Spec	Weight	Pass/Fail
IEEE_ASUSB:five_t_ota_cl_tb:1	GBW	5.028M			

LG GBW

- Compare DC gain and GBW with those obtained from open-loop simulation. Comment.

Quantity	OL sim results	LG sim results
DC gain	37.3dB	37.3dB
GBW	5MHZ	5MHZ

As the feedback loop is built in unity gain configuration, $\beta = 1$ and thus $LG = \beta A_{OL} = A_{OL}$. This justifies the equality between A_{OL} and LG and the BW of both quantities.

- Compare simulation results with hand calculations in a table.

<i>Quantity</i>	<i>Simulated</i>	<i>Calculated</i>
<i>DC gain</i>	<i>37.3dB</i>	<i>37.3dB</i>
<i>GBW</i>	<i>5MHZ</i>	<i>5.12MHz</i>

Exactly the same as OL Calculations as $\beta = 1$ and is frequency independent, thus it has no ability to make any difference between A_{OL} and LG.